

学号:

姓名:

年级、专业、班级:

学院:


线 封 密

山东大学电气工程学院电路 (2) 期末考试(A卷) 2024 ~ 2025学年第一学期


注意事项	1. 答题前请先将姓名、学号填涂清楚。	学号(*必填项*)																				
	2. 客观题使用2B铅笔填涂; 修改时用橡皮擦干净。	<table border="1" style="width: 100%; height: 20px;"> <tr> <td></td><td></td><td></td><td></td><td></td><td></td><td></td><td></td><td></td><td></td><td></td><td></td> </tr> </table>																				
填涂	3. 请严格按照题号在相应答题区域作答, 超出答题区域的答案无效; 在草稿纸、试卷上答题无效。禁止填涂答题纸四角的识别区。	[0]	[0]	[0]	[0]	[0]	[0]	[0]	[0]	[0]	[0]	[0]										
	4. 保持卷面清洁, 不要装订、折叠、破损。	[1]	[1]	[1]	[1]	[1]	[1]	[1]	[1]	[1]	[1]	[1]										
考生禁填	正确填涂: <input type="checkbox"/> 错误填涂: <input type="checkbox"/> <input type="checkbox"/> <input type="checkbox"/> <input type="checkbox"/> <input type="checkbox"/>	[2]	[2]	[2]	[2]	[2]	[2]	[2]	[2]	[2]	[2]	[2]										
	缺考 <input type="checkbox"/>	[3]	[3]	[3]	[3]	[3]	[3]	[3]	[3]	[3]	[3]	[3]										
	作弊 <input type="checkbox"/>	[4]	[4]	[4]	[4]	[4]	[4]	[4]	[4]	[4]	[4]	[4]										
	违纪 <input type="checkbox"/>	[5]	[5]	[5]	[5]	[5]	[5]	[5]	[5]	[5]	[5]	[5]										
		[6]	[6]	[6]	[6]	[6]	[6]	[6]	[6]	[6]	[6]	[6]										
	[7]	[7]	[7]	[7]	[7]	[7]	[7]	[7]	[7]	[7]	[7]											
	[8]	[8]	[8]	[8]	[8]	[8]	[8]	[8]	[8]	[8]	[8]											
	[9]	[9]	[9]	[9]	[9]	[9]	[9]	[9]	[9]	[9]	[9]											

电路 (2) 期末考试答题纸


1. (15分)

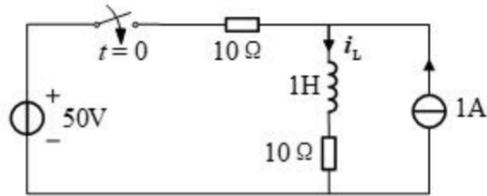


2. (10分)

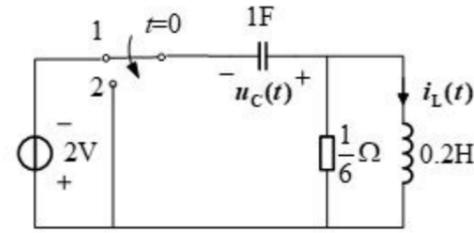


3. (15分)

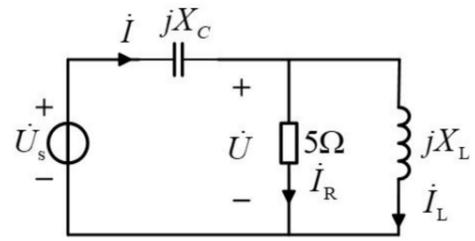


4. (10分)

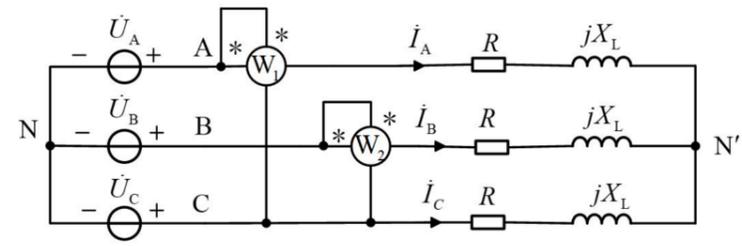


5. (15分)

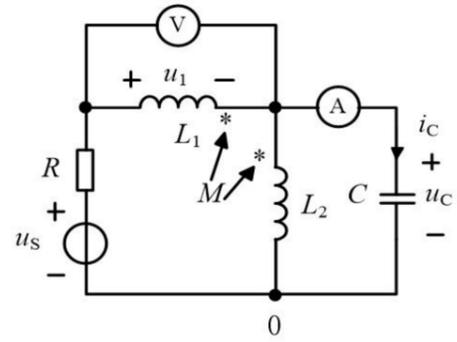

6. (10分)

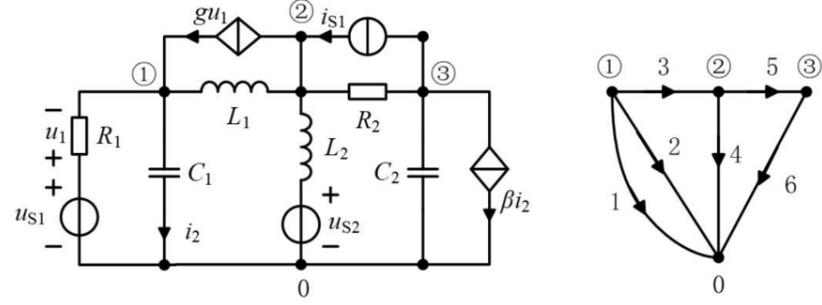

7. (10分)

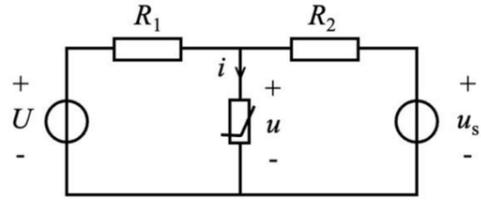

8. (15分)

